

The background of the slide features a series of fluid, overlapping waves in shades of purple, magenta, and pink. These waves flow horizontally across the frame, creating a sense of movement and depth. The colors transition from a deep purple on the left to a lighter pink on the right, with various translucent layers creating a complex, ethereal pattern.

TASK 2

APPROACHES TO CONVERT 220V AC TO 24V DC

- Using a 220V AC → 24V DC (2A) Adapter

- Pros :

- Simple , requires only connecting
 - Stable 24V DC output
 - Compact and space-saving

- Cons :

- Internal settings (protection/limits) cannot be adjusted
 - Expensive
 - Not customizable

- Using a Transformer + Filtering Circuit

- Pros :


- Fully customizable design, adjusted to use with any load
 - Can be lower cost depending on design

- Cons :

- Requires more complex wiring
 - Must include safety margin to ensure output stays near 24V

• IDEA BEHIND THE DESIGN

- Following the second approach, I built a fully customizable AC to DC converter, with load control using a 5V signal. The design includes isolation to protect components from common issues such as:
 - Voltage spikes from the AC source
 - Inductive spikes caused by switching
- In the next sections, each part of the circuit will be discussed in detail, including its working principle and relevant calculations.

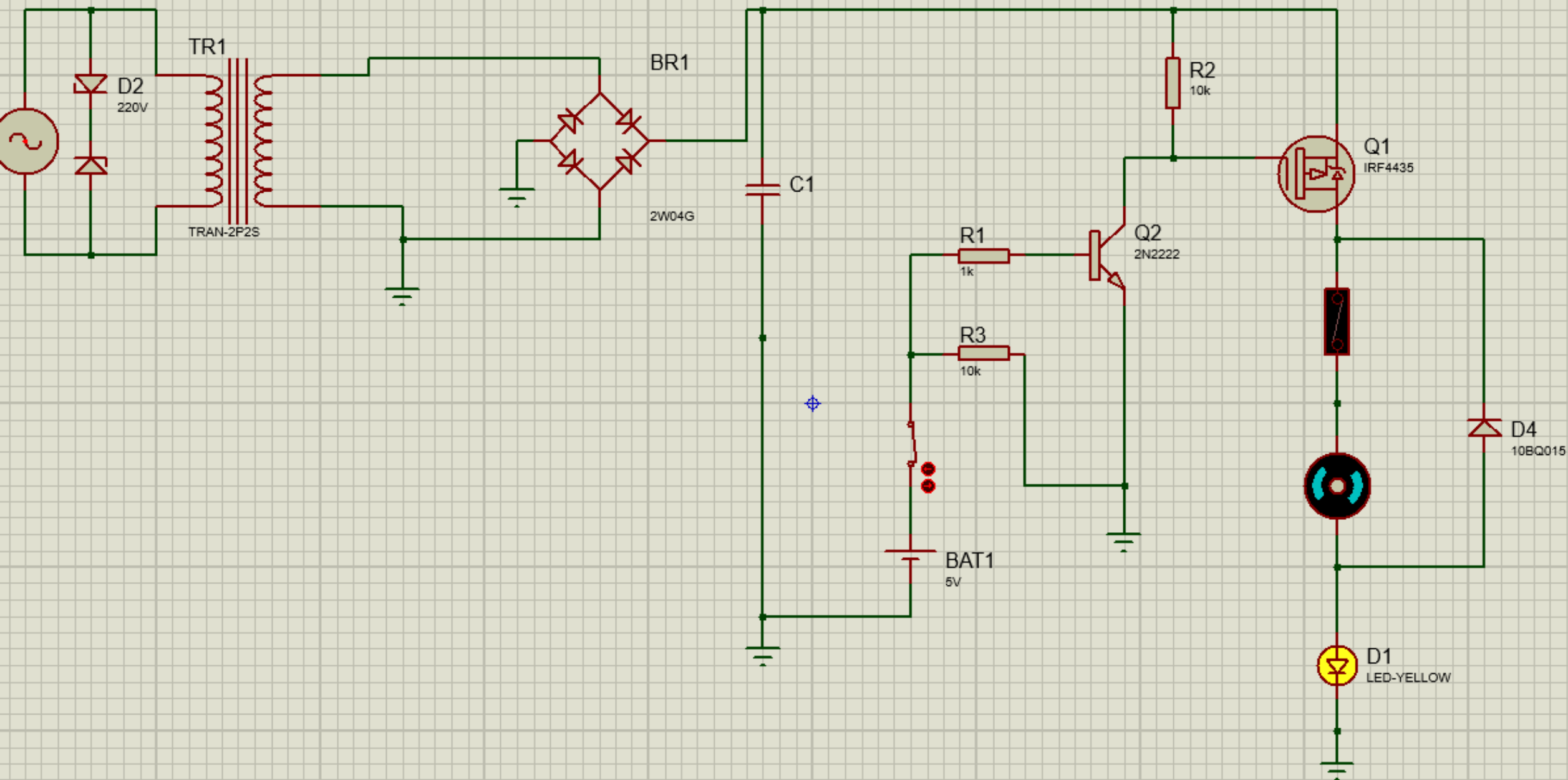


STEPPING DOWN

[1] A step down transformer

- Designed with a primary/secondary inductance ratio of **148**
- Based on ($v_p/v_s = \sqrt{\frac{L_p}{L_s}}$)
- Steps 220V AC down to **~18.08V AC_25.57Vmax_**, accounting for voltage drops

[2] Zener diodes

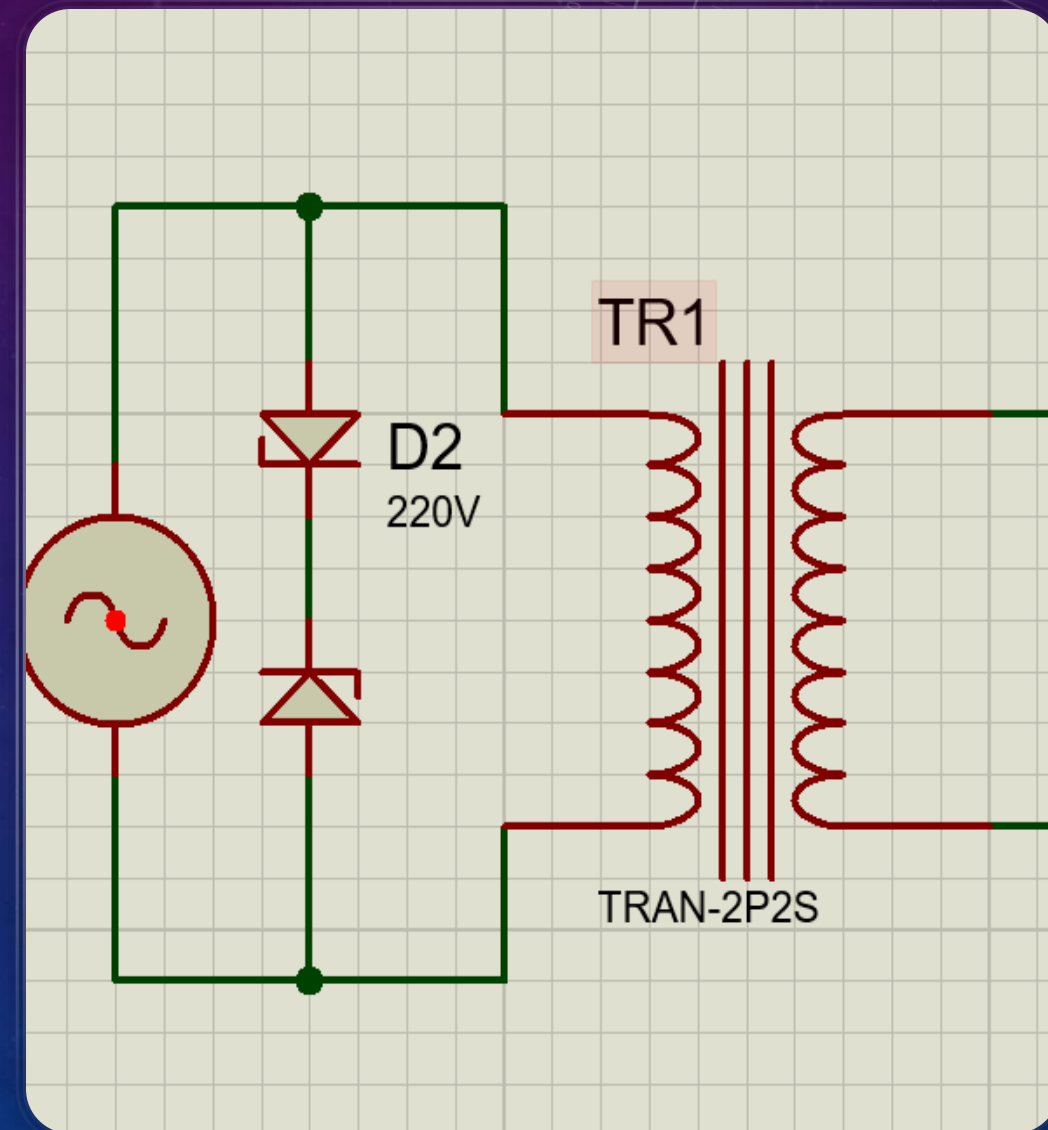- Added to **suppress voltage spikes**
- Limit the input voltage to **220V max**



FILTERING


[3] Full bridge rectifier

- rectifies the signal
- more efficient than HWR in filtering (higher Vdc and frequency)

$$-V_m = v_{sec} - 1,4(\text{loss in diodes}) = 24.17V$$

[4] Capacitor

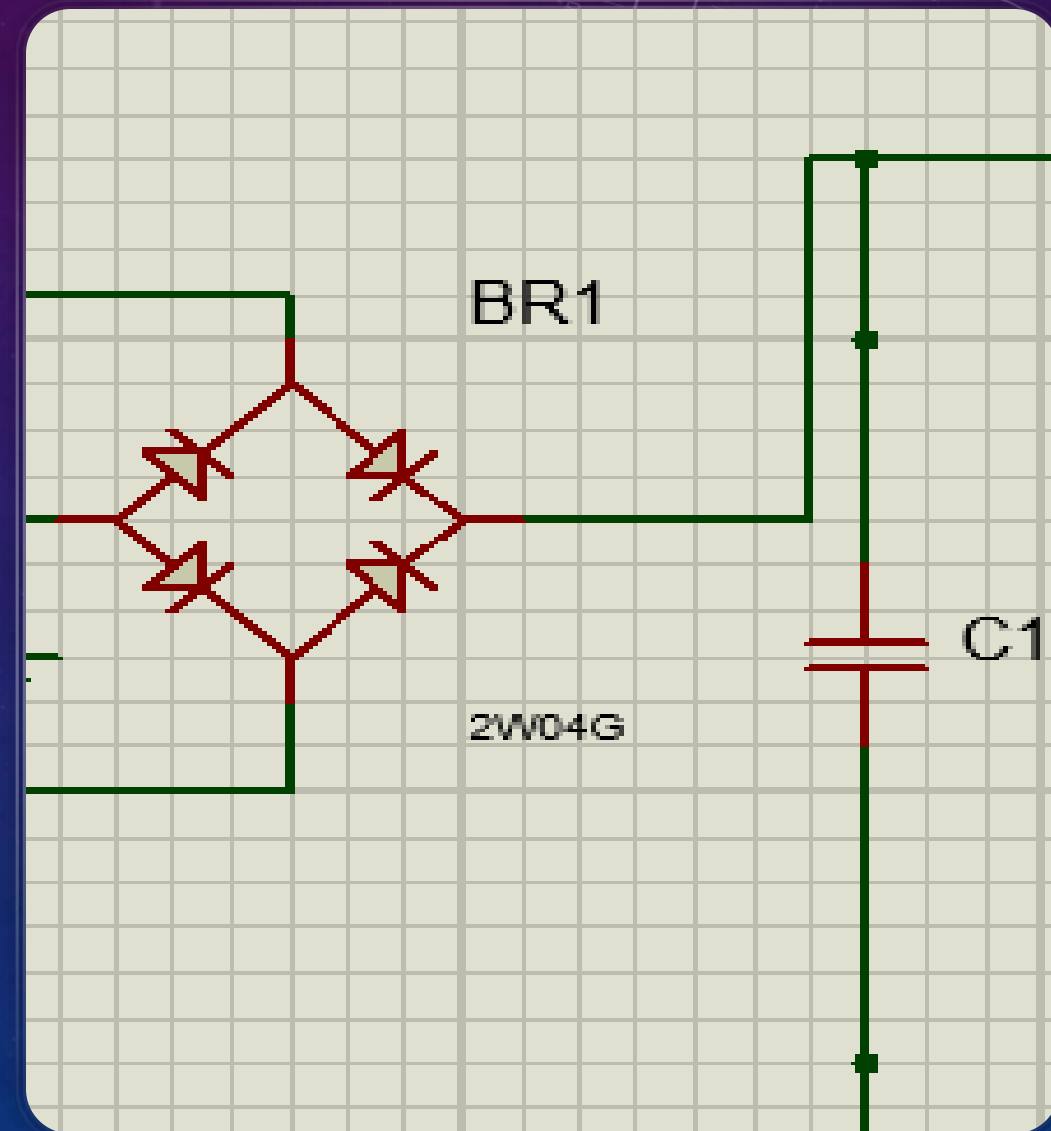- The higher the capacity the better the filtering based on
$$v_{ripple} = \frac{v_m}{F * C * R}$$
- 30000 uf would result in maximum ripple of 0.33 without accounting for the load resistance (12 ohm -> 0.0277 ripple)



LOAD CONTROL

[5] MOSFET

– Acts as the high-side


- Off when $V_G = V_S$
- On when V_G is pulled low switch for the motor:

[6] Transistor

– Level-shifts the 5 V logic to drive the MOSFET gate:

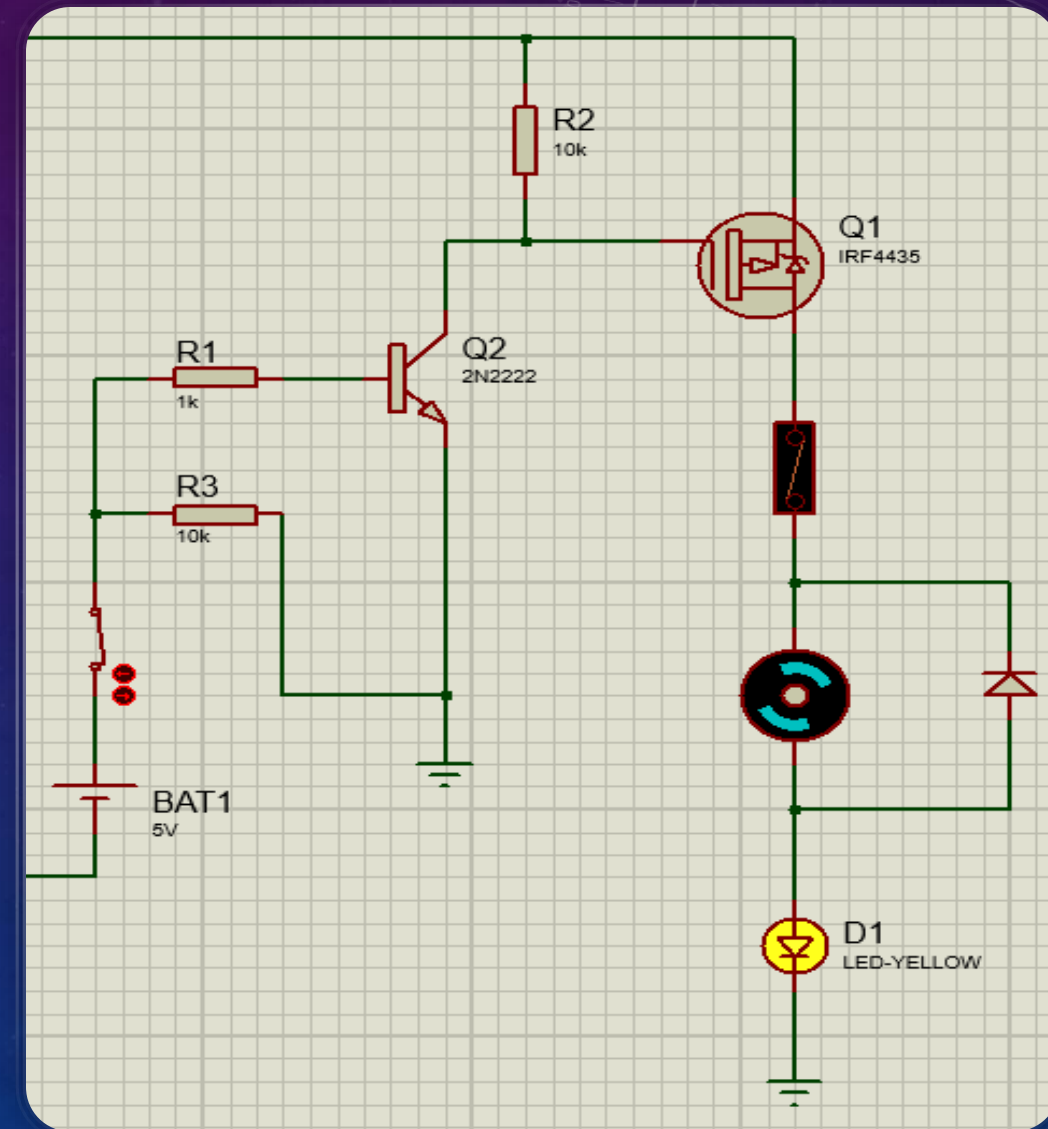- Q2 only conducts when $V_{IN} > V_{BE}$ (~ 0.7 V), so small noise spikes won't turn it on
- When 5 V is present, Q2 saturates and pulls the gate to 0 V
- When 5 V is absent, Q2 is off and R2 (10 k Ω) pulls the gate up to 24 V

– The V_{BE} threshold provides inherent noise immunity; for even stricter “5 V only” switching you can add a diode or small cap on the base to sharpen the turn-on edge




LOAD PROTECTION

[7] Fuse

- Protects the motor against currents above 2A

[8] Diode

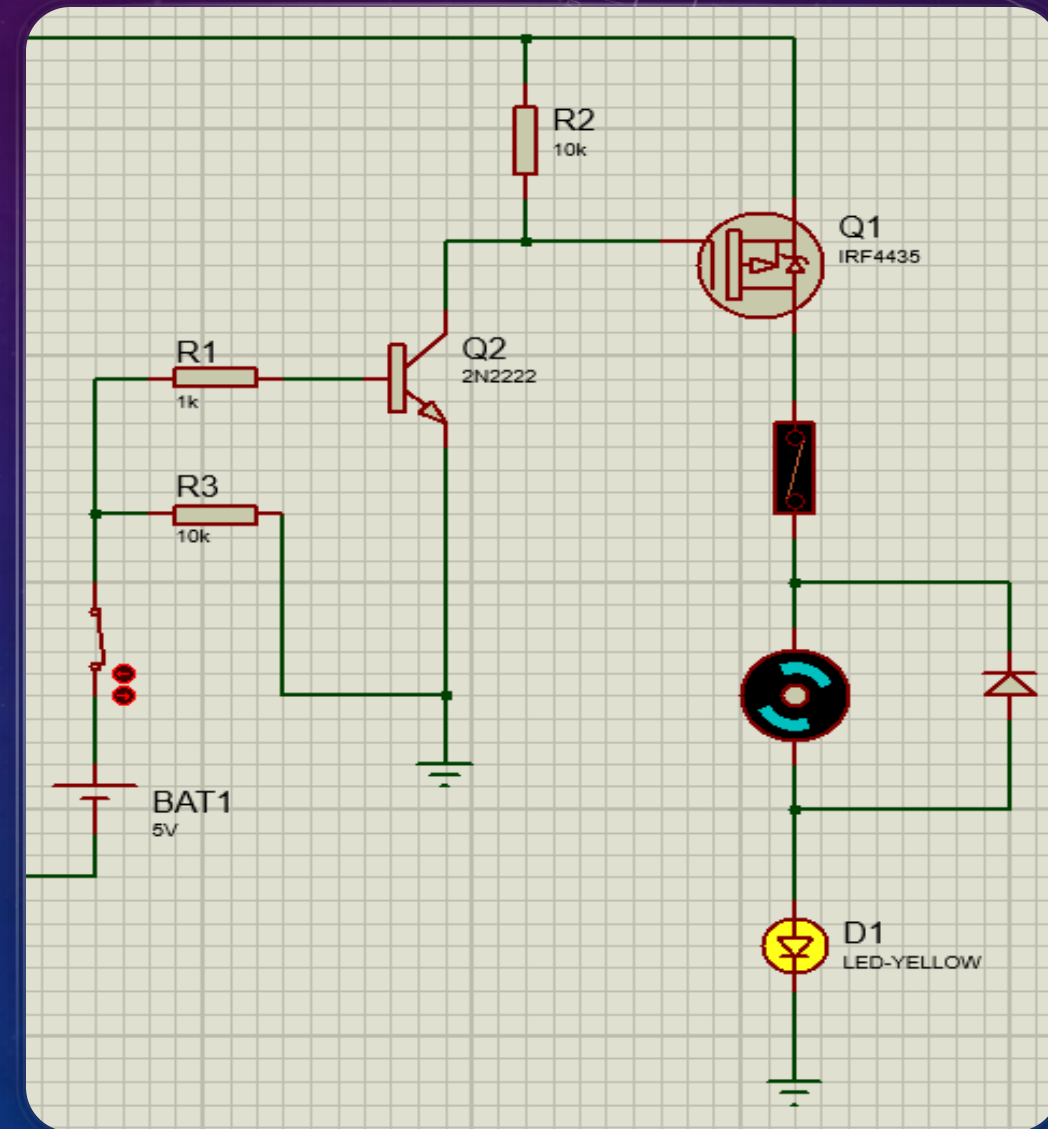- a parallel diode to protect the load against inductive spikes when turning on and off



• COMPONENTS LIST

- [1] A step down transformer <https://makerselectronics.com/product/transformer-220v-18v-0-18v-2a/>
- [2] Zener diodes <https://eu.mouser.com/ProductDetail/Vishay-Semiconductors/BZT03C220-TR?qs=yIvI1B2wDi5PnCFRIEdTug%3D%3D>
- [3] Bridge Rectifier <https://makerselectronics.com/product/kbp310-bridge-rectifier-single-phase-3a-1000v-kbp-3/>
- [4] Capacitor <https://makerselectronics.com/product/capacitor-10000uf-25v/>,
[https://makerselectronics.com/?s=Capacitor+10000uF&post_type=product&type_aws=true_higher voltage reating_](https://makerselectronics.com/?s=Capacitor+10000uF&post_type=product&type_aws=true_higher+voltage+reating_)
- [5] MOSFET <https://makerselectronics.com/product/irf5305-p-channel-power-mosfet/>
- [6] Transistor <https://makerselectronics.com/product/2n2222-npn-bipolar-transistor-to-92/?srsltid=AfmBOorky8ROIIQvZzZKDBB-F59rn8hUrCcQOKfq-K9LY0OpdQEr32jk>
- [7] FUSE https://makerselectronics.com/?s=FUSE&post_type=product&type_aws=true